

Unit-2: Model-checker NuSMV

B. Srivathsan

Chennai Mathematical Institute

NPTEL-course

July - November 2015



Module 3:

Hardware verification using NuSMV




$$y = \text{NOT}(\text{XOR}(x, r))$$

$$r_{\text{next}} = \text{XOR}(x, r)$$

  

$$y = \text{NOT}(\text{XOR}(x, r))$$

$$r_{\text{next}} = \text{XOR}(x, r)$$

 


```
MODULE main
```


```
VAR
```

```
  x: boolean;
```

```
  r: boolean;
```

 

$$y = \text{NOT}(\text{XOR}(x, r))$$
 
$$r_{\text{next}} = \text{XOR}(x, r)$$


```
MODULE main
```


```
VAR
```

```
  x: boolean;
```

```
  r: boolean;
```


```
ASSIGN
```

```
  init(r) := FALSE;
```

 

$y = \text{NOT}(\text{XOR}(x, r))$

$r_{\text{next}} = \text{XOR}(x, r)$

 


MODULE main

VAR

x: boolean;

r: boolean;

 



ASSIGN

init(r) := FALSE;

next(r) := x xor r;

$y = \text{NOT}(\text{XOR}(x, r))$

$r_{\text{next}} = \text{XOR}(x, r)$

  

```
MODULE main
```

```
VAR
```

```
  x: boolean;
```

```
  r: boolean;
```

```
DEFINE
```

```
  y := !(x xor r);
```

```
ASSIGN
```

```
  init(r) := FALSE;
```

```
  next(r) := x xor r;
```


Simple circuit

Use of DEFINE





```
MODULE main
```

```
VAR
```

```
    in1:  boolean;
```

```
    in2:  boolean;
```

```
DEFINE
```

```
    -- ZERO DELAY
```

```
    out := !(in1 & in2);
```



0
0
1

0
1
1

1
0
1

1
1
0

```
MODULE main
```

```
VAR
```

```
    in1: boolean;
```

```
    in2: boolean;
```

```
DEFINE
```

```
    -- ZERO DELAY
```

```
    out := !(in1 & in2);
```



```
MODULE main
```

```
VAR
```


```
    in1: boolean;
```

```
    in2: boolean;
```

```
DEFINE
```

```
    -- ZERO DELAY
```

```
    out := !(in1 & in2);
```

 

```
MODULE main
```

```
VAR
```

```
    in1: boolean;
```

```
    in2: boolean;
```

```
DEFINE
```

```
    -- ZERO DELAY
```

```
    out := !(in1 & in2);
```



```
MODULE main
```

```
VAR
```

```
    in1: boolean;
```

```
    in2: boolean;
```

```
    out: boolean;
```

```
ASSIGN
```

```
    -- UNIT DELAY
```

```
    init(out) := TRUE;
```

```
    next(out) := !(in1 & in2);
```



0
0
0

0
0
1 ←

0
1
0

0
1
1 ←

1
0
0

1
0
1 ←

1
1
0

1
1
1 ←

MODULE main

VAR

in1: boolean;

in2: boolean;


out: boolean;

ASSIGN

-- UNIT DELAY

init(out) := TRUE;

next(out) := !(in1 & in2);

 

```
MODULE main
```

```
VAR
```

```
    in1: boolean;
```

```
    in2: boolean;
```


```
    out: boolean;
```

```
ASSIGN
```

```
    -- UNIT DELAY
```

```
    init(out) := TRUE;
```

```
    next(out) := !(in1 & in2);
```

 

```
MODULE main
```

```
VAR
```

```
    in1: boolean;
```

```
    in2: boolean;
```


```
    out: boolean;
```

```
ASSIGN
```

```
    -- UNIT DELAY
```

```
    init(out) := TRUE;
```

```
    next(out) := !(in1 & in2);
```

 

```
MODULE main
```

```
VAR
```

```
    in1: boolean;
```

```
    in2: boolean;
```


```
    out: boolean;
```

```
ASSIGN
```

```
    -- UNIT DELAY
```

```
    init(out) := TRUE;
```

```
    next(out) := !(in1 & in2);
```

 

```
MODULE main
```

```
VAR
```

```
    in1: boolean;
```

```
    in2: boolean;
```


```
    out: boolean;
```

```
ASSIGN
```

```
    -- UNIT DELAY
```

```
    init(out) := TRUE;
```

```
    next(out) := !(in1 & in2);
```

 

```
MODULE main
```

```
VAR
```

```
    input1: boolean;
```

```
    input2: boolean;
```

```
    q: nand2(input1, input2);
```

```
MODULE nand2(in1, in2)
```

```
VAR
```


```
    out: boolean;
```

```
ASSIGN
```

```
    -- UNIT DELAY
```

```
    init(out) := TRUE;
```


```
    next(out) := !(in1 & in2);
```

 

```

MODULE main
VAR
    x1:  boolean; x2:boolean;
    y1:  boolean; y2:boolean;
    q1:  nand2(x1, x2);
    q2:  nand2(y1, y2);
DEFINE
    -- ZERO DELAY
    fout := q1.out xor q2.out;

 MODULE nand2(in1, in2)
VAR
    out:  boolean;
ASSIGN
    -- UNIT DELAY
    init(out) := TRUE;
    next(out) := !(in1 & in2);
  
```



```

MODULE main
VAR
    x:  boolean;
    y:  boolean;
    q1: nand2(x, q2.out);
    q2: nand2(q1.out, y);
DEFINE
    -- ZERO DELAY
    fout := q1.out xor q2.out;

MODULE nand2(in1, in2)
VAR
    out: boolean
ASSIGN
    -- UNIT DELAY
    init(out) := TRUE;
    next(out) := !(in1 & in2);

```

Simple circuit

Use of DEFINE


Hierarchical designs

Use of MODULE




```
MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

 MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);
```



```
MODULE counter_cell(carry_in)
```

```
VAR
```

```
    value:boolean;
```

```
ASSIGN
```

```
    init(value):=FALSE;
```

```
    next(value):= value xor carry_in;
```

```
DEFINE
```

```
    carry_out := carry_in & value;
```


```
MODULE main
```

```
VAR
```

```
    bit0:counter_cell(TRUE);
```

```
    bit1:counter_cell(bit0.carry_out);
```


```
    bit2:counter_cell(bit1.carry_out);
```
 
```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

 
MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);
  
```



```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

 
MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);
  
```



```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

 
MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);
  
```



```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

 
MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);
  
```



```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

 MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);
  
```





```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);

```

 


```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);

```

 


```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);

```

 


```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);

```

 


```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);

```

 


```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);

```

 


```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);

```

 


```

MODULE counter_cell(carry_in)
VAR
    value:boolean;
ASSIGN
    init(value):=FALSE;
    next(value):= value xor carry_in;
DEFINE
    carry_out := carry_in & value;

MODULE main
VAR
    bit0:counter_cell(TRUE);
    bit1:counter_cell(bit0.carry_out);
    bit2:counter_cell(bit1.carry_out);

```
 
```
MODULE counter_cell(carry_in)
```

```
VAR
```

```
    value:boolean;
```

```
ASSIGN
```

```
    init(value):=FALSE;
```

```
    next(value):= value xor carry_in;
```

```
DEFINE
```

```
    carry_out := carry_in & value;
```

```
MODULE main
```

```
VAR
```

```
    bit0:counter_cell(TRUE);
```

```
    bit1:counter_cell(bit0.carry_out);
```

```
    bit2:counter_cell(bit1.carry_out);
```

bit2	bit1	bit0	
	0	0	1 — carry_in
0	0	0	0 — value
			0 — carry_out
	0	1	1
0	0	0	0
	0	0	1
	0	0	1
0	0	0	0
	0	0	1
0	0	1	0
	1	1	1
0	0	1	1
	0	0	1
0	1	0	0
	0	1	1
0	1	0	0
	0	0	1
0	1	0	0
	1	1	1
1	1	1	1

```
MODULE counter_cell(carry_in)
```

```
VAR
```

```
    value:boolean;
```

```
ASSIGN
```

```
    init(value):=FALSE;
```

```
    next(value):= value xor carry_in;
```

```
DEFINE
```

```
    carry_out := carry_in & value;
```


```
MODULE main
```


```
VAR
```


```
    bit0:counter_cell(TRUE);
```


```
    bit1:counter_cell(bit0.carry_out);
```

 
```
    bit2:counter_cell(bit1.carry_out);
```




 


 


 

 

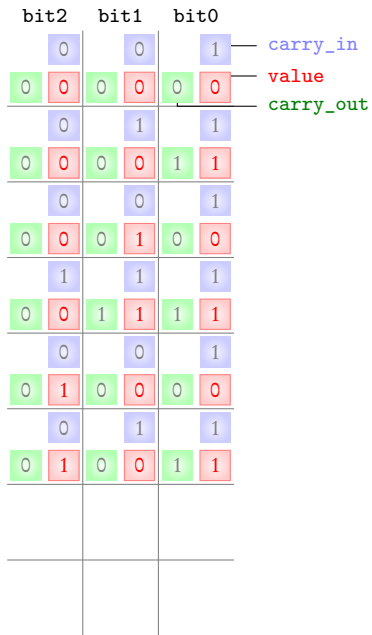

 

 

bit2	bit1	bit0	
	0	0	1 — carry_in
0	0	0	0 — value
			0 — carry_out
	0	1	1
0	0	0	0
	0	0	1
0	0	1	0
	1	1	1
0	0	0	1
0	1	0	0
	1	1	1
0	0	0	1
0	1	0	1
	1	1	1
1	1	1	1

Synchronous composition

All assignments to all MODULES occur simultaneously

(more about this later)

Simple circuit

Use of DEFINE

Hierarchical designs

Use of MODULE

Counter

Synchronous composition
of modules