

# An “Electric” Story of a Drunkard

Ramprasad Saptharishi

Chennai Mathematical Institute  
Third Year B.Sc Mathematics

September 1, 2006

## Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

## 1 Introduction

## 2 Some Electrical Networks and their Effective Resistance

## 3 Connection between Electrical Networks and Random Walks

## 4 Proving Polya's Theorem

## 5 Conclusion

# The Problem Statement

## Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

**Random Walk:** You are placed at some point in a  $d$ -dimensional integer lattice.

*Repeat* {

Pick one of your neighbours uniformly at random  
and move to them

}

# The Problem Statement

## Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

**Random Walk:** You are placed at some point in a  $d$ -dimensional integer lattice.

*Repeat* {

Pick one of your neighbours uniformly at random  
and move to them

}

Question: What is the probability that you return to the starting point infinitely often?

# The Theorem of Polya

## Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

## Theorem

*A random walk on an  $d$ -dimensional integer lattice will return to the starting point infinitely often with probability 1 if  $d = 1$  or 2. The probability is 0 if  $d \geq 3$ .*

# The Theorem of Polya

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

## Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

## Theorem

*A random walk on an  $d$ -dimensional integer lattice will return to the starting point infinitely often with probability 1 if  $d = 1$  or 2. The probability is 0 if  $d \geq 3$ .*

**Drunkard:** Will I ever get home again?

**Polya:** You can't miss, just keep walking, and stay out of 3D!!!

# Structure of this Talk

## Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

- Establish certain electrical networks

# Structure of this Talk

## Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

- Establish certain electrical networks
- Estimate the effective resistance of the electrical networks

# Structure of this Talk

## Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

- Establish certain electrical networks
- Estimate the effective resistance of the electrical networks
- Show the relation between electrical parameters of the networks and random walks

# Structure of this Talk

## Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

- Establish certain electrical networks
- Estimate the effective resistance of the electrical networks
- Show the relation between electrical parameters of the networks and random walks
- Use the effective resistance of networks to prove Polya's theorem.

# Ohm...Kirchoffāya Namahā

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

## Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

**Ohm's Law:** The current flowing through a wire is directly proportional to potential across it.


**Kirchoff's Law:** Current in = current out, for any point in the interior of the circuit.

Net potential drop across a loop is zero

# Outline

- 1 Introduction
- 2 Some Electrical Networks and their Effective Resistance
- 3 Connection between Electrical Networks and Random Walks
- 4 Proving Polya's Theorem
- 5 Conclusion

# Circuit 1

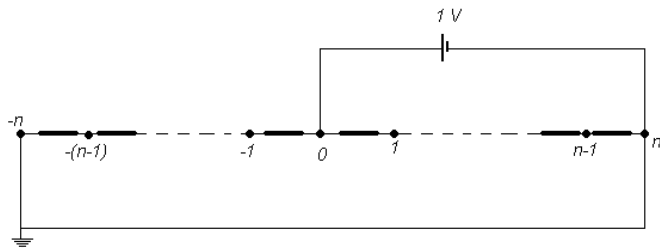

Introduction


Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion


# Circuit 1

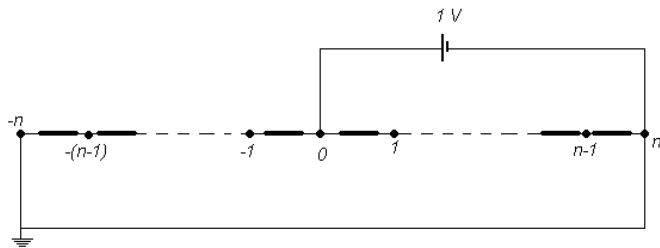

Effective Resistance

$$\rho_n = \frac{rn}{2}$$

# Circuit 1

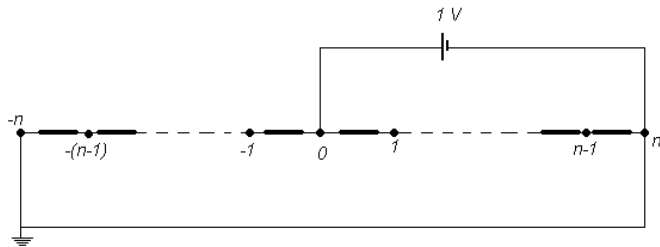

Effective Resistance

$$\rho_n = \frac{rn}{2}$$

$$\rho_n \rightarrow \infty \text{ as } n \rightarrow \infty$$


Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

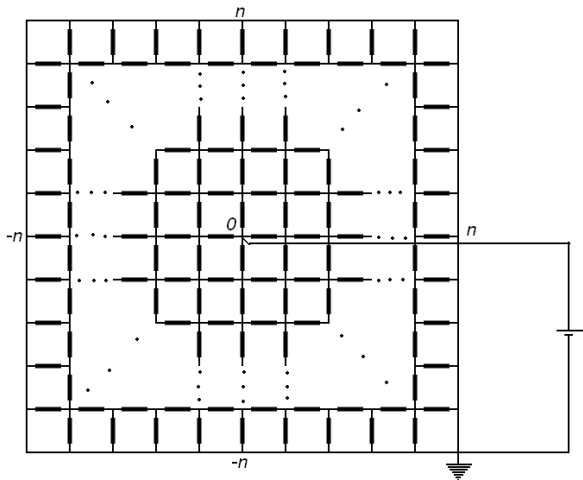

# Hard to calculate? Estimate growth

Difficult to find a closed form answer

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

# Hard to calculate? Estimate growth

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

Difficult to find a closed form answer

But what happens to  $\rho_n$  as  $n \rightarrow \infty$ ?

# Hard to calculate? Estimate growth

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion


Difficult to find a closed form answer

But what happens to  $\rho_n$  as  $n \rightarrow \infty$ ?


Find an easier circuit with effective resistance  $\rho' < \rho$  and see if you can show that  $\rho'$  is infinite.
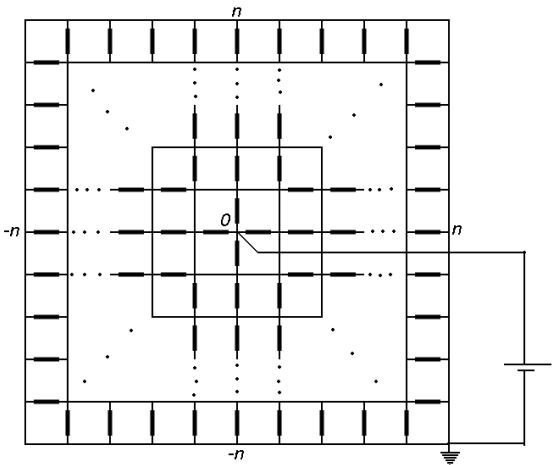
# An Easier Circuit

- Introduction
- Some Electrical Networks and their Effective Resistance
- Connection between Electrical Networks and Random Walks
- Proving Polya's Theorem
- Conclusion



...which is equivalent to

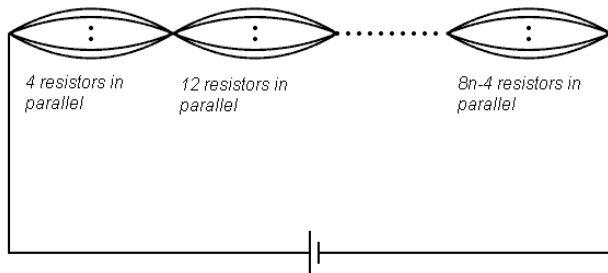

Introduction


Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem


Conclusion

...which is equivalent to

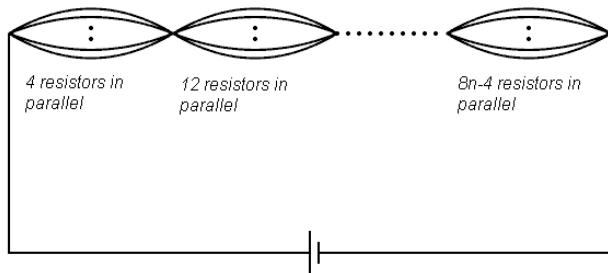

$$\rho'_n = \sum_{k=1}^n \frac{r}{8k-4}$$


...which is equivalent to

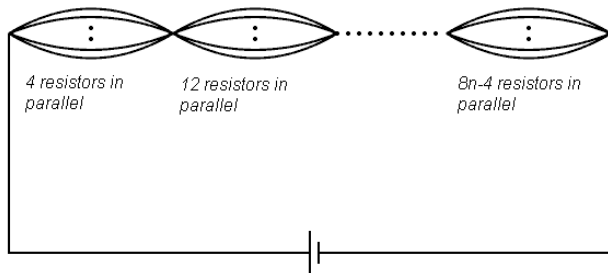

$$\rho'_n = \sum_{k=1}^n \frac{r}{8k-4}$$

Hence, we have  $\rho'_n \rightarrow \infty$  as  $n \rightarrow \infty$

...which is equivalent to

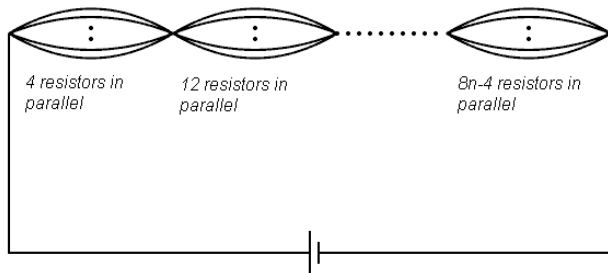

$$\rho'_n = \sum_{k=1}^n \frac{r}{8k-4}$$

Hence, we have  $\rho'_n \rightarrow \infty$  as  $n \rightarrow \infty$ , which implies that  $\rho_n \rightarrow \infty$  as  $n \rightarrow \infty$ .

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

## Circuit 3: The $3D$ version

## Circuit 3: The $3D$ version

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

Again, difficult to find a closed form solution

## Circuit 3: The $3D$ version

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

Again, difficult to find a closed form solution

What can you say about  $\rho_n$  as  $n \rightarrow \infty$ ?

## Circuit 3: The 3D version

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

Again, difficult to find a closed form solution

What can you say about  $\rho_n$  as  $n \rightarrow \infty$ ?

*Can you show that it is finite?*

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

# Approach

# Approach

Can't short resistors, won't help in showing that it is finite.

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

# Approach

Can't short resistors, won't help in showing that it is finite.

Remove some resistors, equivalent to saying increase some resistances to infinity

# Approach

Can't short resistors, won't help in showing that it is finite.

Remove some resistors, equivalent to saying increase some resistances to infinity


Show that the effective resistance of the new circuit is bounded.

An "Electric"  
Story of a  
Drunkard


Ramprasad  
Saptharishi
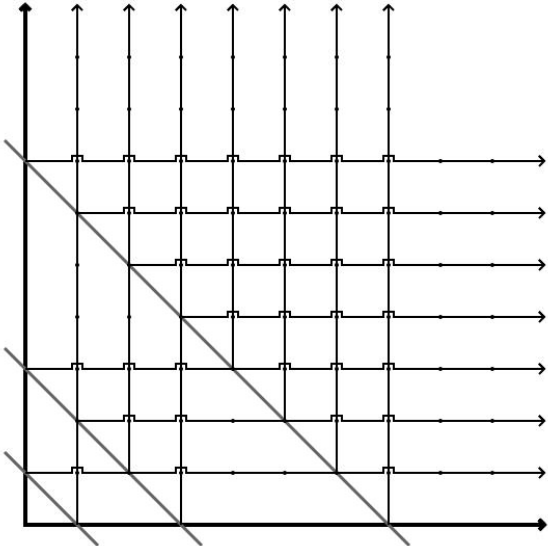
# Getting Back to 2D

- Introduction
- Some Electrical Networks and their Effective Resistance
- Connection between Electrical Networks and Random Walks
- Proving Polya's Theorem
- Conclusion



...which is equivalent to

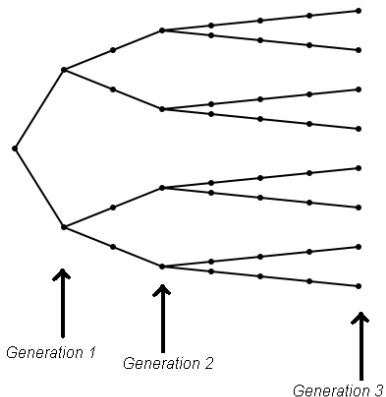

Introduction


Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem


Conclusion

...which is equivalent to

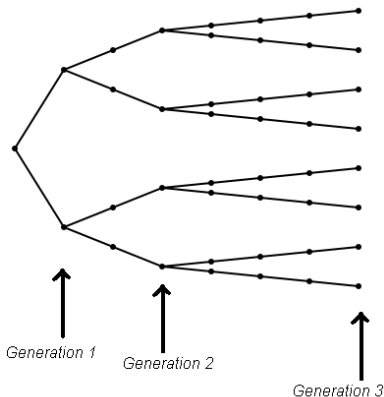

All *Generation i* nodes are of the same potential; can connect them without changing effective resistance.

...which is equivalent to

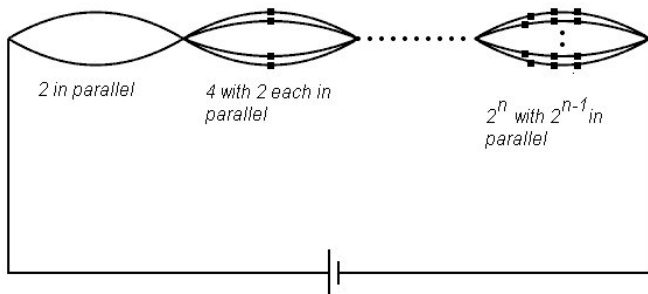

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

# Back to 3D

## Back to 3D

- Take the planes  $x + y + z = 2^i - 1$  and do the same thing.

## Back to 3D

- Take the planes  $x + y + z = 2^i - 1$  and do the same thing.
- Every time a line of resistance hits such a plane, it forks in the  $x$ ,  $y$  and the  $z$  direction.

## Back to 3D

- Take the planes  $x + y + z = 2^i - 1$  and do the same thing.
- Every time a line of resistance hits such a plane, it forks in the  $x$ ,  $y$  and the  $z$  direction.
- Establish the tree again


Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance


Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

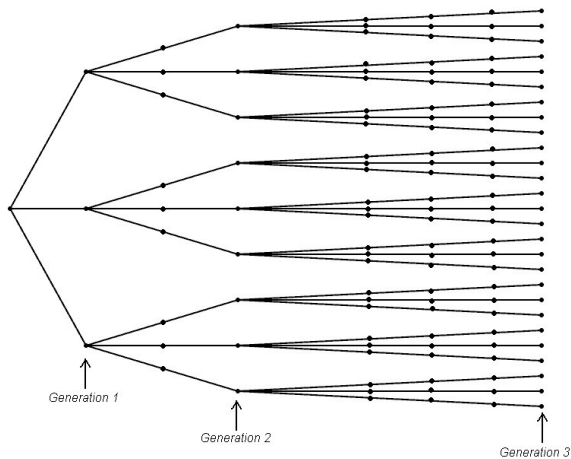

...which is equivalent to

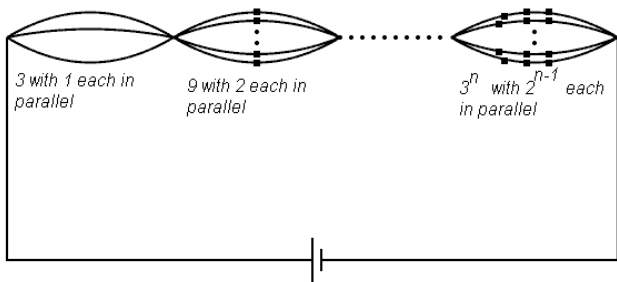

## Effective resistance

$$\begin{aligned}\rho'_n &= \frac{r}{3} + \frac{2r}{9} + \dots + \frac{2^{n-1}r}{3^n} \\ &= \left(1 - \left(\frac{2}{3}\right)^n\right)r\end{aligned}$$

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

## Effective resistance

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

$$\begin{aligned}\rho'_n &= \frac{r}{3} + \frac{2r}{9} + \dots + \frac{2^{n-1}r}{3^n} \\ &= \left(1 - \left(\frac{2}{3}\right)^n\right)r\end{aligned}$$

$$\therefore \lim_{n \rightarrow \infty} \rho'_n = r$$

## Effective resistance

$$\begin{aligned}\rho'_n &= \frac{r}{3} + \frac{2r}{9} + \dots + \frac{2^{n-1}r}{3^n} \\ &= \left(1 - \left(\frac{2}{3}\right)^n\right) r\end{aligned}$$

$$\therefore \lim_{n \rightarrow \infty} \rho'_n = r$$

Hence  $\rho$  for circuit 3 is finite.

## Circuit $d$ : $d > 3$

- Use the same approach, draw the corresponding planes
- Branch whenever it the lines hit the plane

## Circuit $d$ : $d > 3$

- Use the same approach, draw the corresponding planes
- Branch whenever it the lines hit the plane

?????

## Circuit $d$ : $d > 3$

- Use the same approach, draw the corresponding planes
- Branch whenever it the lines hit the plane

?????

Finite for  $d = 3 \Rightarrow$  finite for  $d > 3$

# Outline

- 1 Introduction
- 2 Some Electrical Networks and their Effective Resistance
- 3 Connection between Electrical Networks and Random Walks**
- 4 Proving Polya's Theorem
- 5 Conclusion

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

## 2 'different' problems

## 2 'different' problems

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

- Let  $G$  be a graph, with two special nodes  $\alpha, \beta$ . Suppose we start at some node  $x$ , what is the probability  $p(x)$  that a simple random walk starting from  $x$  reaches  $\alpha$  before  $\beta$ .

## 2 'different' problems

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

- Let  $G$  be a graph, with two special nodes  $\alpha, \beta$ . Suppose we start at some node  $x$ , what is the probability  $p(x)$  that a simple random walk starting from  $x$  reaches  $\alpha$  before  $\beta$ .
- Take that graph, put a resistance of  $r$  on every edge in the graph. Give  $\alpha$  a potential of 1, and  $\beta$  a potential of 0. What is the potential of the point  $x$ ?

## 2 'different' problems

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

- Let  $G$  be a graph, with two special nodes  $\alpha, \beta$ . Suppose we start at some node  $x$ , what is the probability  $p(x)$  that a simple random walk starting from  $x$  reaches  $\alpha$  before  $\beta$ .
- Take that graph, put a resistance of  $r$  on every edge in the graph. Give  $\alpha$  a potential of 1, and  $\beta$  a potential of 0. What is the potential of the point  $x$ ?

**Claim:** Both are the same!

## Some Notations

- $R_{xy}$  : Resistance of the edge  $\{x, y\}$
- $C_{xy}$  : Conductance of the edge, defined as  $\frac{1}{R_{xy}}$
- $C_x$  : Conductance of the vertex, defined as  $\sum_{y \in \Gamma(x)} C_{xy}$
- $i_{xy}$  : Current through the edge  $\{x, y\}$
- $v(x)$  : Potential at the point  $x$
- $i_\alpha$  : Net current flowing through the circuit

## Some Equations

$$i_{xy} = \frac{v(y) - v(x)}{R_{xy}} = (v(y) - v(x)) C_{xy}$$

## Some Equations

$$i_{xy} = \frac{v(y) - v(x)}{R_{xy}} = (v(y) - v(x)) C_{xy}$$

Summing over all neighbours  $y$  of  $x$

$$\sum_{y \in \Gamma(x)} v(x) C_{xy} = v(x) C_x = \sum_{y \in \Gamma(x)} v(y) C_{xy}$$

## Some Equations

$$i_{xy} = \frac{v(y) - v(x)}{R_{xy}} = (v(y) - v(x)) C_{xy}$$

Summing over all neighbours  $y$  of  $x$

$$\sum_{y \in \Gamma(x)} v(x) C_{xy} = v(x) C_x = \sum_{y \in \Gamma(x)} v(y) C_{xy}$$

$$v(x) = \sum_{y \in \Gamma(x)} v(y) \frac{C_{xy}}{C_x}$$

## Some Equations

$$i_{xy} = \frac{v(y) - v(x)}{R_{xy}} = (v(y) - v(x)) C_{xy}$$

Summing over all neighbours  $y$  of  $x$

$$\sum_{y \in \Gamma(x)} v(x) C_{xy} = v(x) C_x = \sum_{y \in \Gamma(x)} v(y) C_{xy}$$

$$v(x) = \sum_{y \in \Gamma(x)} v(y) \frac{C_{xy}}{C_x}$$

And of course,  $v(\alpha) = 1, v(\beta) = 0$ .

# Defining Equations for $p(x)$

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

$$P(x) = \begin{cases} \frac{1}{\# \text{ of vertices adjacent to } x} & \text{if } y \text{ adjacent to } x \\ 0 & \text{otherwise} \end{cases}$$

... the probability that you reach  $y$  from  $x$  in 1 step.

# Defining Equations for $p(x)$

Now we have:

$$p(x) = \sum_{y \in \Gamma(x)} p(y)P_{xy}; p(\alpha) = 1; p(\beta) = 1$$

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

# Defining Equations for $p(x)$

Now we have:

$$p(x) = \sum_{y \in \Gamma(x)} p(y)P_{xy}; p(\alpha) = 1; p(\beta) = 1$$

Hey, this looks familiar...

## Defining Equations for $p(x)$

Now we have:

$$p(x) = \sum_{y \in \Gamma(x)} p(y) P_{xy}; p(\alpha) = 1; p(\beta) = 1$$

Hey, this looks familiar...

$$v(x) = \sum_{y \in \Gamma(x)} v(y) \frac{C_{xy}}{C_x}; v(\alpha) = 1; v(\beta) = 0$$

Bingo!

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

If,

$$P_{xy} = \frac{C_{xy}}{C_x}$$

then we have

$$p(x) = v(x)$$

Bingo!

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

If,

$$P_{xy} = \frac{C_{xy}}{C_x}$$

then we have

$$p(x) = v(x)$$

...connection established!

# Outline

- 1 Introduction
- 2 Some Electrical Networks and their Effective Resistance
- 3 Connection between Electrical Networks and Random Walks
- 4 Proving Polya's Theorem
- 5 Conclusion

# What are we looking for?

We are interested in finding the probability that we return to the starting point  $\alpha$  before reaching  $\beta$

# What are we looking for?

We are interested in finding the probability that we return to the starting point  $\alpha$  before reaching  $\beta$

This is as good as saying, we go out  $\alpha$ , then get back from there to  $\alpha$  before reaching  $\beta$ .

## What are we looking for?

We are interested in finding the probability that we return to the starting point  $\alpha$  before reaching  $\beta$

This is as good as saying, we go out  $\alpha$ , then get back from there to  $\alpha$  before reaching  $\beta$ .

Thus we are hunting for

$$\xi = \sum_{y \in \Gamma(\alpha)} p(y) P_{\alpha y}$$

# Net Current

$$i_\alpha = \sum_{y \in \Gamma(x)} (v(\alpha) - v(y)) C_{\alpha y}$$

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

# Net Current

$$\begin{aligned}i_{\alpha} &= \sum_{y \in \Gamma(x)} (v(\alpha) - v(y)) C_{\alpha y} \\ &= v(\alpha) \sum_{y \in \Gamma(x)} C_{\alpha y} - \sum_{y \in \Gamma(x)} v(y) C_{\alpha y}\end{aligned}$$

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

## Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

$$\begin{aligned}i_{\alpha} &= \sum_{y \in \Gamma(x)} (v(\alpha) - v(y)) C_{\alpha y} \\ &= v(\alpha) \sum_{y \in \Gamma(x)} C_{\alpha y} - \sum_{y \in \Gamma(x)} v(y) C_{\alpha y} \\ &= C_{\alpha} - C_{\alpha} \sum_{y \in \Gamma(x)} p(y) P_{\alpha y}\end{aligned}$$

## Net Current

$$\begin{aligned}i_{\alpha} &= \sum_{y \in \Gamma(x)} (v(\alpha) - v(y)) C_{\alpha y} \\&= v(\alpha) \sum_{y \in \Gamma(x)} C_{\alpha y} - \sum_{y \in \Gamma(x)} v(y) C_{\alpha y} \\&= C_{\alpha} - C_{\alpha} \sum_{y \in \Gamma(x)} p(y) P_{\alpha y} \\&= C_{\alpha} \left( 1 - \sum_{y \in \Gamma(x)} p(y) P_{xy} \right)\end{aligned}$$

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

$$\begin{aligned}i_{\alpha} &= \sum_{y \in \Gamma(x)} (v(\alpha) - v(y)) C_{\alpha y} \\&= v(\alpha) \sum_{y \in \Gamma(x)} C_{\alpha y} - \sum_{y \in \Gamma(x)} v(y) C_{\alpha y} \\&= C_{\alpha} - C_{\alpha} \sum_{y \in \Gamma(x)} p(y) P_{\alpha y} \\&= C_{\alpha} \left( 1 - \sum_{y \in \Gamma(x)} p(y) P_{xy} \right)\end{aligned}$$

$$\therefore \sum_{y \in \Gamma(x)} p(y) P_{xy} = \xi = 1 - \frac{i_{\alpha}}{C_{\alpha}}$$

## Net Current

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

$$\begin{aligned}i_{\alpha} &= \sum_{y \in \Gamma(x)} (v(\alpha) - v(y)) C_{\alpha y} \\&= v(\alpha) \sum_{y \in \Gamma(x)} C_{\alpha y} - \sum_{y \in \Gamma(x)} v(y) C_{\alpha y} \\&= C_{\alpha} - C_{\alpha} \sum_{y \in \Gamma(x)} p(y) P_{\alpha y} \\&= C_{\alpha} \left( 1 - \sum_{y \in \Gamma(x)} p(y) P_{xy} \right)\end{aligned}$$

$$\therefore \sum_{y \in \Gamma(x)} p(y) P_{xy} = \xi = 1 - \frac{i_{\alpha}}{C_{\alpha}} = 1 - \frac{1}{\rho C_{\alpha}}$$

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

Thus...

$$\xi = 1 - \frac{1}{\rho C_\alpha}$$

Thus...

$$\xi = 1 - \frac{1}{\rho C_\alpha}$$

For  $d = 1$  or  $2$ , we have  $\rho = \infty$  and hence  $\xi = 1$ .

$$\therefore \lim_{n \rightarrow \infty} \xi^n = 1$$

Thus...

$$\xi = 1 - \frac{1}{\rho C_\alpha}$$

For  $d = 1$  or  $2$ , we have  $\rho = \infty$  and hence  $\xi = 1$ .

$$\therefore \lim_{n \rightarrow \infty} \xi^n = 1$$

For  $d \geq 3$ , we have a finite  $\rho$  and hence  $0 < \xi < 1$ .

$$\therefore \lim_{n \rightarrow \infty} \xi^n = 0$$

Thus...

$$\xi = 1 - \frac{1}{\rho C_\alpha}$$

For  $d = 1$  or  $2$ , we have  $\rho = \infty$  and hence  $\xi = 1$ .

$$\therefore \lim_{n \rightarrow \infty} \xi^n = 1$$

For  $d \geq 3$ , we have a finite  $\rho$  and hence  $0 < \xi < 1$ .

$$\therefore \lim_{n \rightarrow \infty} \xi^n = 0$$



# Outline

- 1 Introduction
- 2 Some Electrical Networks and their Effective Resistance
- 3 Connection between Electrical Networks and Random Walks
- 4 Proving Polya's Theorem
- 5 Conclusion

# End Notes

An "Electric"  
Story of a  
Drunkard

Ramprasad  
Saptharishi

Introduction

Some  
Electrical  
Networks and  
their Effective  
Resistance

Connection  
between  
Electrical  
Networks and  
Random  
Walks

Proving  
Polya's  
Theorem

Conclusion

In probability jargon, it is said that a simple random walk is recurrent in 2 or lower dimensions, and is transient in 3 or higher dimensions.

The original question was asked and solved by George Polya in a celebrated paper in 1921. This method of looking at the question through electrical networks is based on a monograph by Doyle and Snell, where besides the question of transience and recurrence, many other questions of simple random walks are addressed.

# Thank You

Slides and TeX files are available at  
`~ramprasad/studenttalks/drun kard/`.